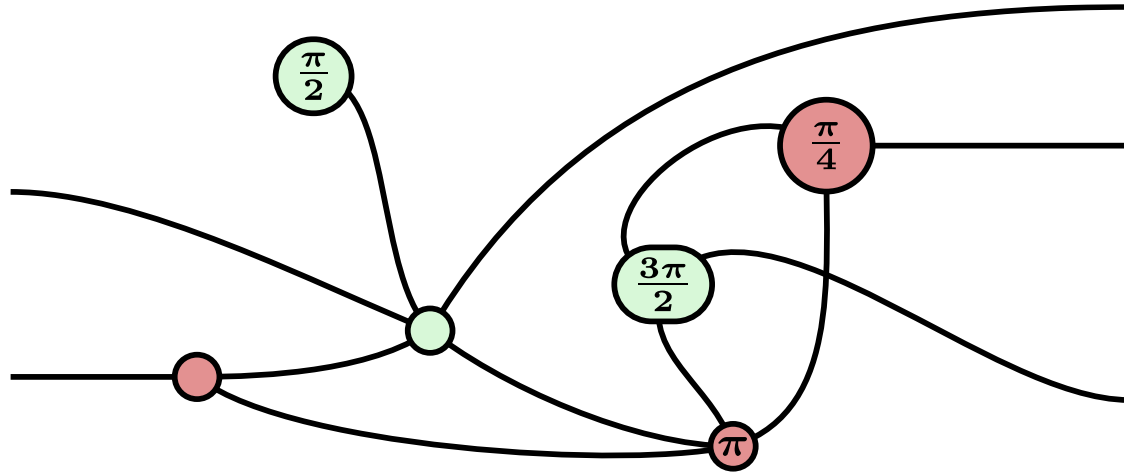


# ZX-Calculus



Manuel Lerchner

11.06.2023


# What is ZX-Calculus?

- A graphical language extending circuit diagrams
  - Allows breaking up logic gates into smaller *atoms*
  - The resulting graph is a *low-level* representation of the circuit
- Using transformations on those atoms we can visually deduce
  - Properties of circuits
  - Entangled states
  - How quantum protocols work

- Quantum circuit optimization
  - Reduce complexity of circuits
  - T-count reduction
    - Important metric for performing fault tolerant computations
- Circuit Compilation
  - Reducing high level quantum algorithms to run on a target architecture

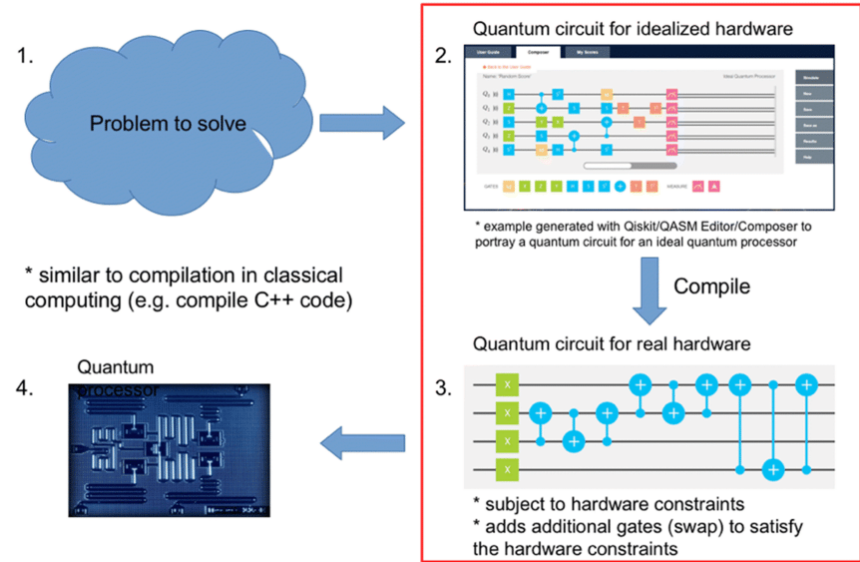
# Quantum Circuit optimization

- Circuits use many abstract gates
- Problems of real quantum computers:
  - Limited set of gates
  - Limited connectivity between qubits
  - Noise
- Special circuit transformations
  - To swap qubits, so they can be entangled
  - Reduce depth of circuit (noise issues)
  - Allow only some set of gates
- ZX-Calculus can solve this
  - Can try to stick to those rules during the reconstruction phase





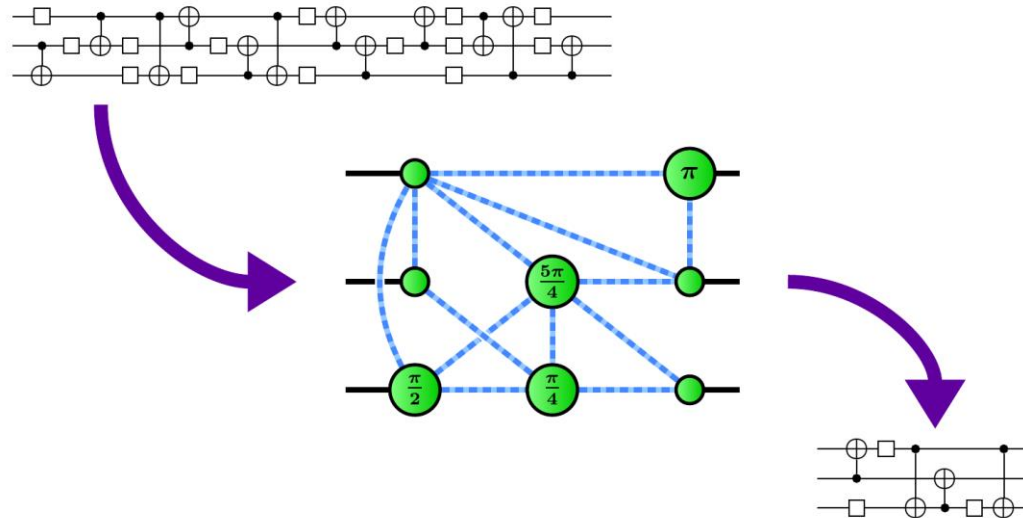
# Quantum Circuit optimization

- Goal: Transform circuits into equivalent circuits
  - New Circuit must have fewer / simpler gates



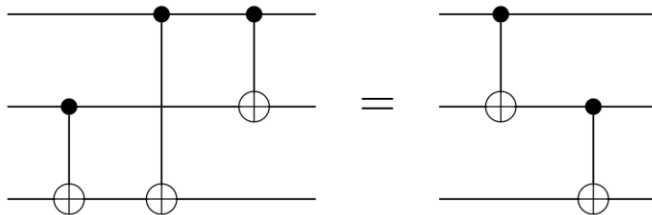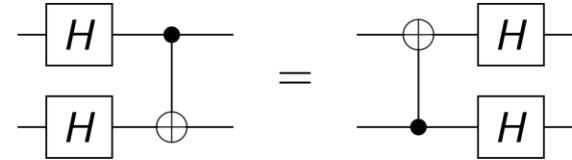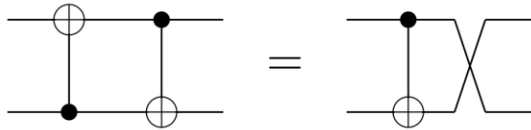
# Classical optimization

- Why use ZX-Calculus for this?
- Circuit simplifications also exist for logic gates:



# Classical optimization

- Unfortunately, there are more ...

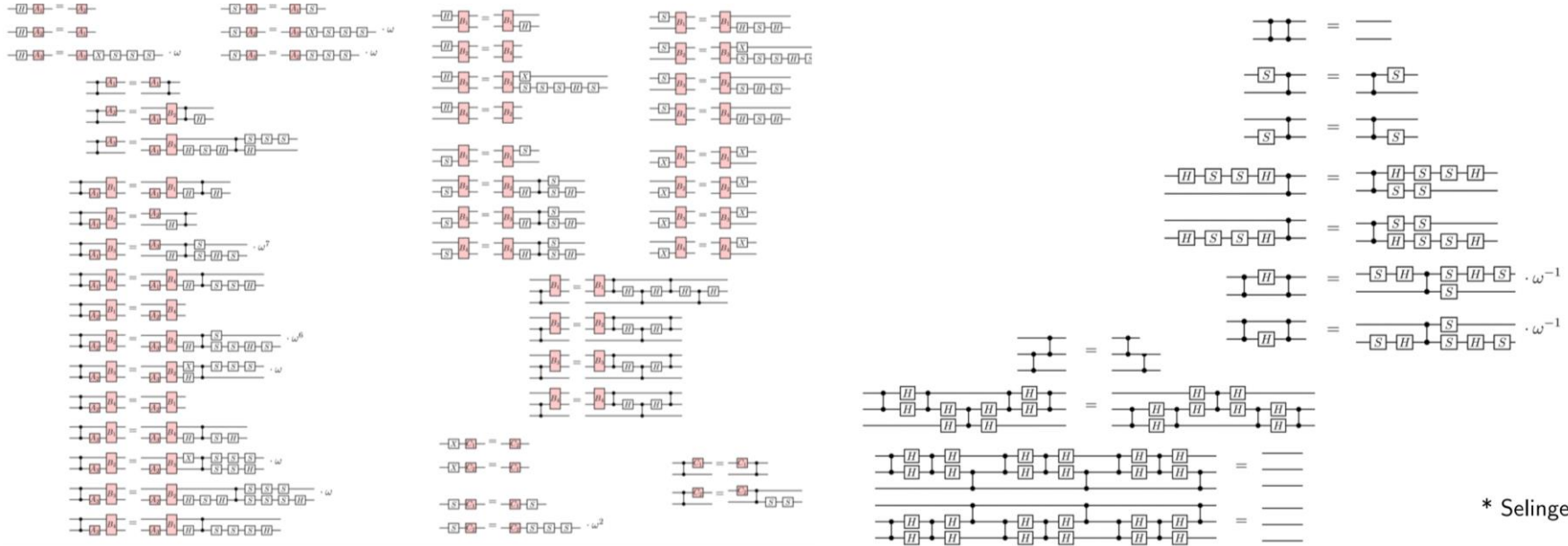

\* Selinger 2015


- 
- Quantum circuit diagrams illustrating various transformations and optimizations, including gates like  $H$ ,  $P$ ,  $P^\dagger$ ,  $R_z$ ,  $R'_z$ ,  $T$ , and  $T^\dagger$ .
- \* Nam et al 2019

\* Nam *et al* 2018



# Classical optimization

- And even more ...

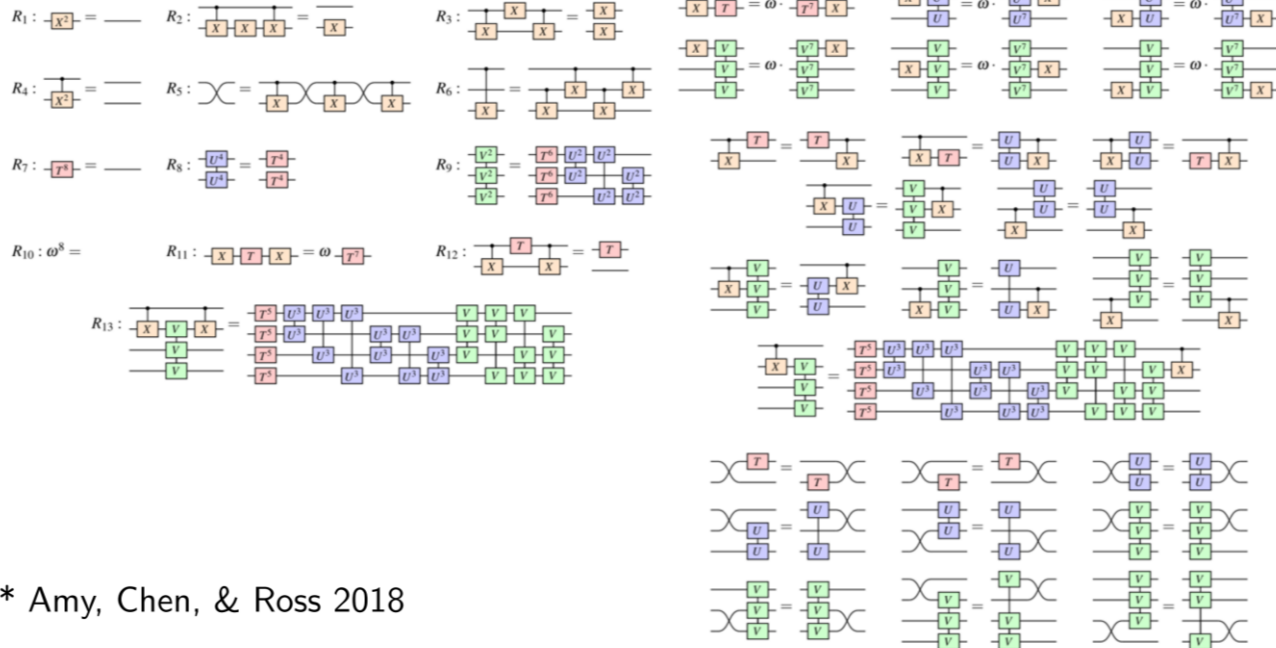


\* Amy, Chen, & Ross 2018

- Optimizing a circuit classically is unpractical
  - Finding an optimal simplification path is hard
  - Huge number of identities to consider
- ZX-Calculus solves this problem
  - It has a massively reduced set of simplification rules
  - Finding the optimal path is still hard, but its manageable
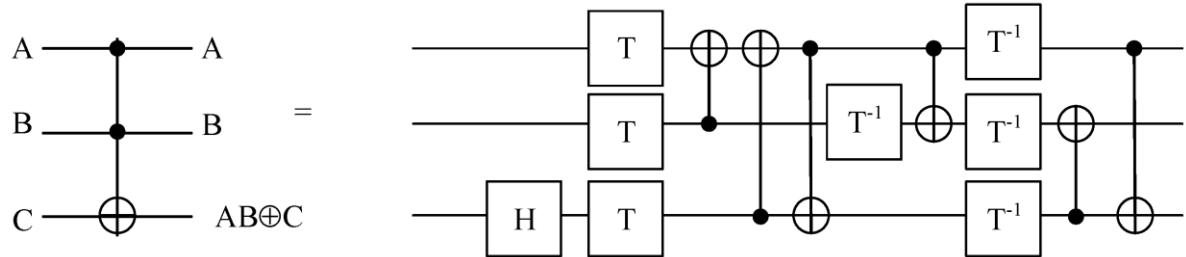
# T-Count Optimization


- Quantum computers are affected by noise
- Clifford+T Circuits can be made tolerant to noise
  - Problem: Many new T-Gates need to be introduced
  - Difficult to simulate (Hardware Limits, high latency)
- ZX-Calculus can simplify such circuits



Decomposition of a Toffoli Gate: TCount = 7
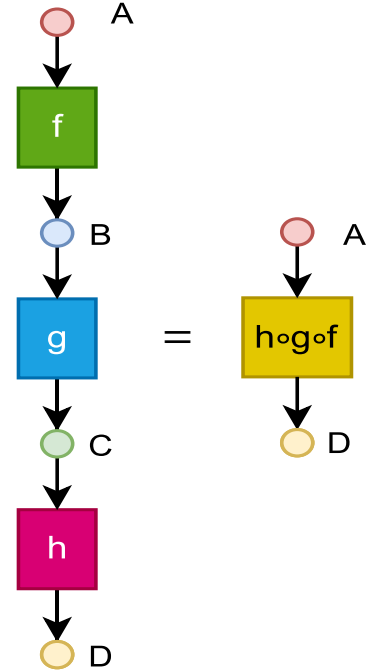
# Mathematical Background: Category Theory

- Category  $\mathcal{C}$  consists of **objects** and **arrows** (/morphisms)
  - Objects:  $\{A, B, C, D\}$
  - Morphisms:  $f: A \rightarrow B$ ,  $g: B \rightarrow C$ ,  $h: C \rightarrow D$
- Every object  $A$  has an identity function
  - $id_A: A \rightarrow A$
  - Represent *loops* in the diagram
- Naturally there exists an associative Composition ( $\circ$ )
  - Which is just the application of  $f$  and then  $g$  in a sequence
  - Example:  $g \circ f: A \rightarrow C$
  - Composition with  $id$  does nothing
    - $id_B \circ f = f \circ id_A = f: A \rightarrow B$



$$h \circ g \circ f: A \rightarrow D$$

# Extension: Monoidal Category

- Extend a Category  $\mathcal{C}$  with:



- An associative Bifunctor:  $\otimes: \mathcal{C} \times \mathcal{C} \rightarrow \mathcal{C}$
- A special object  $I \in \text{obj}(\mathcal{C})$  with
  - $A \otimes I = A \otimes I = A$  for all objects  $A$

- Example:

- For the morphisms:  $f: A \rightarrow B$ ,  $g: B \rightarrow C$ ,  $h: C \rightarrow D$
- We can *apply* them in *parallel*
  - $f \otimes g \otimes h: A \otimes B \otimes C \rightarrow B \otimes C \otimes D$


- So far: Very similar to regular circuit calculations

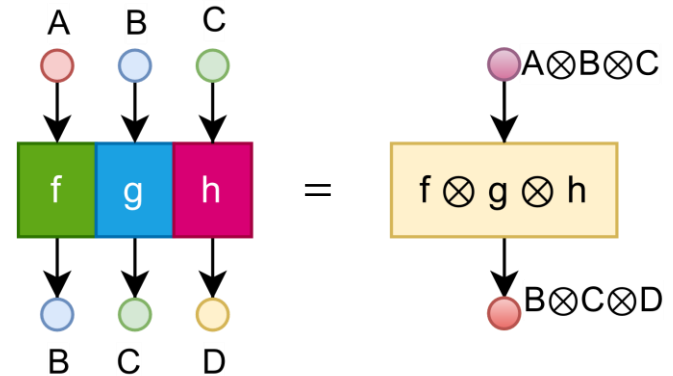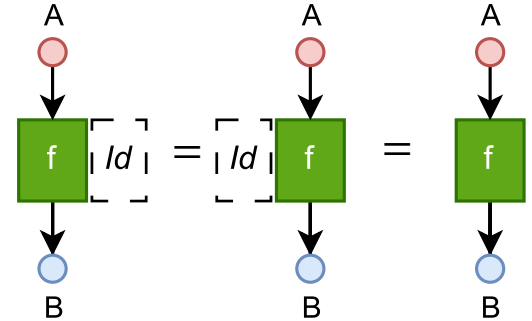- Matrix product for sequential gates
- Tensor product for parallel gates




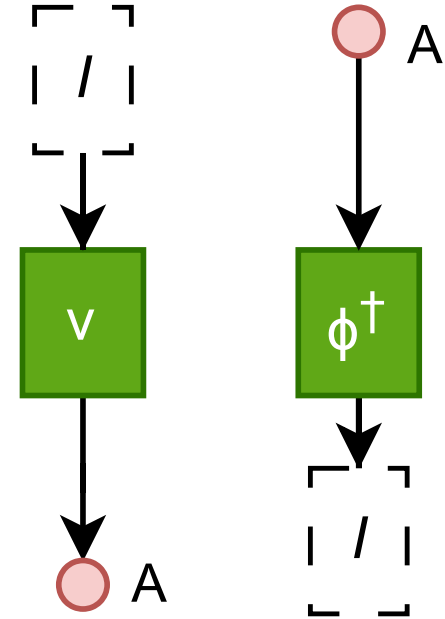
# Special morphisms in Monoidal Categories

- Preparing States:
  - $v: I \rightarrow A$  (Ket)
  - Creates State  $A$  out of nothing
- Erasing States:
  - $\phi^\dagger: A \rightarrow I$  (Bra)
  - Deletes state  $A$


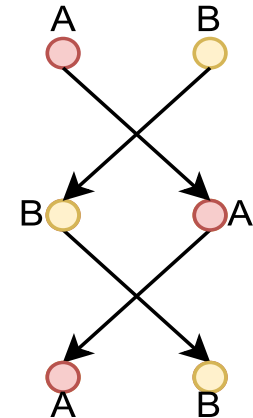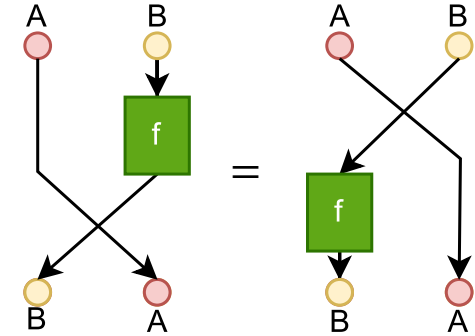
# Extension: Symmetric Monoidal Category


- Extend a Monoidal Category  $\mathcal{C}$  with:
  - Special tensor product: Swap isomorphism
    - $\sigma_{A,B} : A \otimes B \rightarrow B \otimes A$
    - For all  $A, B \in \text{obj}(\mathcal{C})$
- Some other rules must hold:
  - “Push through” rule
  - “Double Swap = Identity” rule




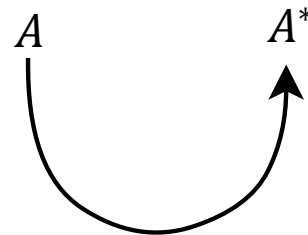
# Extension: Compact Monoidal Category

- If a monoidal category  $\mathcal{C}$  has:
  - A dual object  $A^*$  for every object  $A \in \text{obj}(\mathcal{C})$
  - Special morphisms:
    - *Unit*:  $\eta_A : I \rightarrow A^* \otimes A$
    - *Counit*:  $\epsilon_A : A \otimes A^* \rightarrow I$
- The combining rule must hold:
  - Meaning:  $(\epsilon_A \otimes id_A) \circ (id_A \otimes \eta_A) = id_A$  for all  $A \in \text{obj}(\mathcal{C})$
  - „Push through“ rule also holds
- Why do all this mathematical mess?
  - It can just be seen graphically!
  - Just follow the lines
  - “Only Topology Matters”

$$\epsilon_A : A \otimes A^* \rightarrow I$$




$$\eta_A : I \rightarrow A^* \otimes A$$

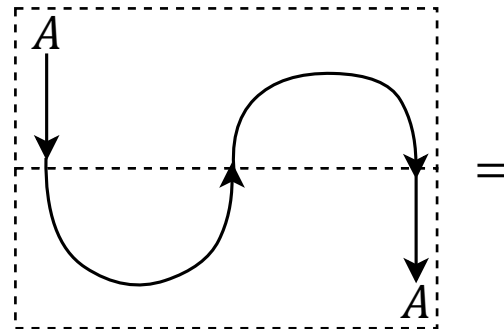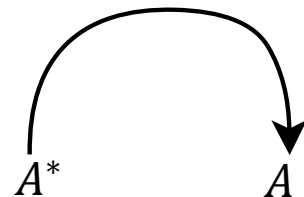




# Example Network

- Concrete Category: **FDHilb**
  - Objects: Hilbert Spaces / (Vector Spaces)
    - Concrete  $I = \mathbb{C}, Q = \mathbb{C}^n$
  - Morphisms: Linear Maps
    - $m = \mathbb{C}^{m \times n}$
  - Tensor Product: Kronecker Product
  - Composition: Matrix Product
- Skeleton of Entanglement Circuit
  1. Create two  $|0\rangle$  States
  2. Apply Hadamard
  3. Apply CNOT


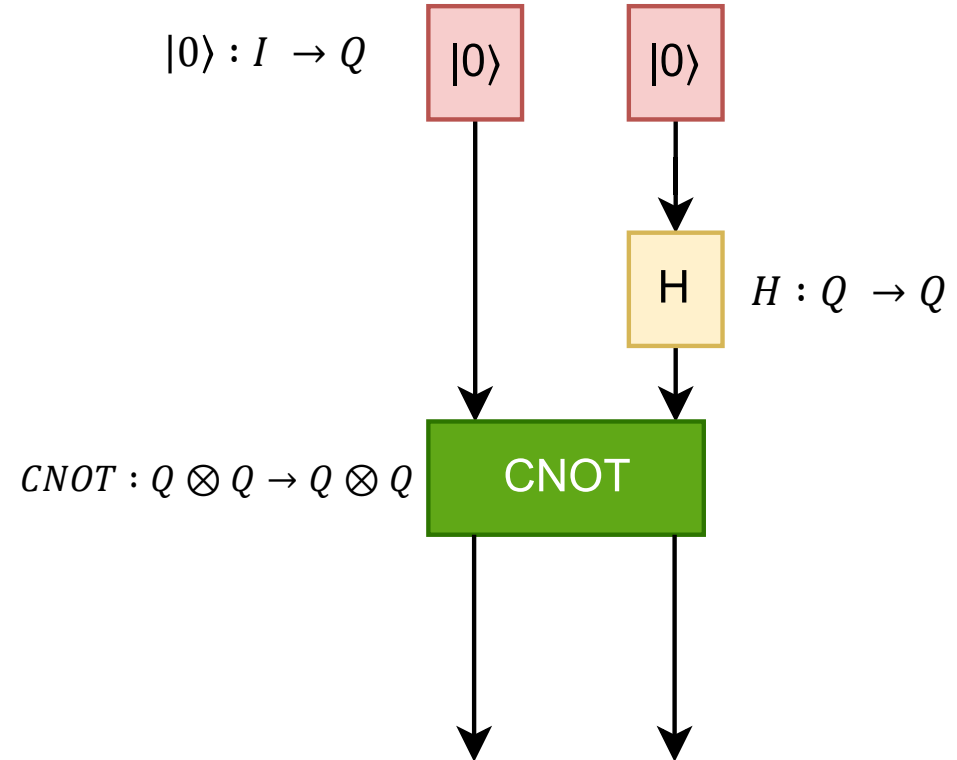


- Main idea of ZX-Calculus
  - Represent quantum circuit visually as network of morphisms
  - Apply simplifications on the network
  - “Only topology Matters”
    - If it looks like the same graph its the same thing
    - Guaranteed by the rules of the underlying Category
- The circuit consists of the *atoms* of logic gates
  - We represent this atoms using spiders
  - Spiders represent the morphisms from before

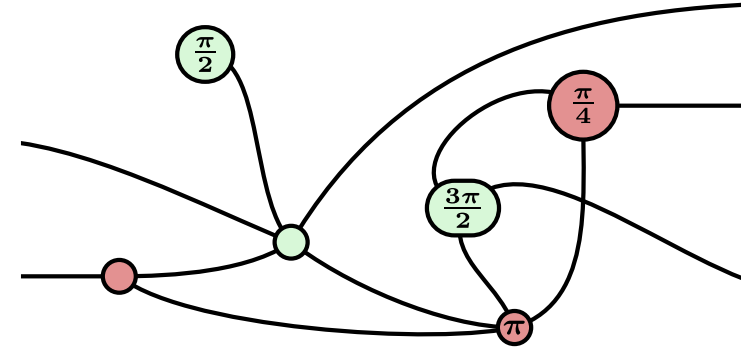
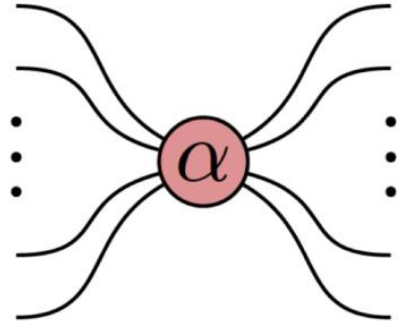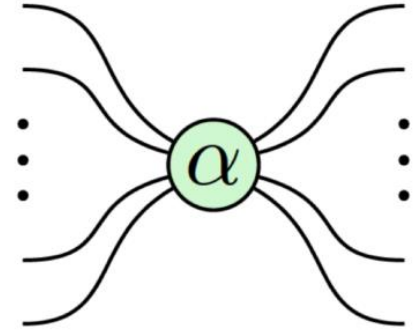
# Spiders

- Spiders are the nodes in the graph
  - Arbitrary number of inputs / outputs
  - Represent linear maps
- Spider variations:
  - Green
    - Defined using with eigenbasis of  $Z$  matrix
  - Red
    - Defined using with eigenbasis of  $X$  matrix
  - Can have a phase angle  $\alpha$



# Spiders as linear maps

- Each spider is a linear map


- $$\text{GreenSpider}(n, m)_{\alpha} = \underbrace{|0 \dots 0\rangle}_{m} \underbrace{\langle 0 \dots 0|}_{n} + e^{i\alpha} \underbrace{|1 \dots 1\rangle}_{m} \underbrace{\langle 1 \dots 1|}_{n}$$

- $$\text{RedSpider}(n, m)_{\alpha} = \underbrace{|+\dots+\rangle}_{m} \underbrace{\langle +\dots+|}_{n} + e^{i\alpha} \underbrace{|-\dots-\rangle}_{m} \underbrace{\langle -\dots-|}_{n}$$

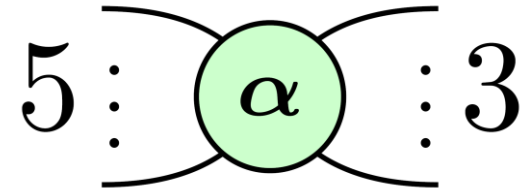- Example Spider:

- $\text{GreenSpider}(5, 3)_{\alpha}$  represents a  $2^3 \times 2^5 = 8 \times 32$  matrix
  - Not unitary
  - Not even square
- Spiders extend classical gates into non-dimensional matrices

$$\left[ \begin{array}{c} \vdots \\ \text{Spider } \alpha \\ \vdots \end{array} \right] = \begin{pmatrix} 1 & 0 & & \\ 0 & 0 & & \\ & & \ddots & \\ & & & 0 & 0 \\ & & & 0 & e^{i\alpha} \end{pmatrix}$$



# Spiders for Basis States

- Spiders can represent States **and** Gates

- Global scalars are omitted

- **X-Basis:**  $GreenSpider(n, m)_\alpha = \underbrace{|0 \dots 0\rangle}_m \underbrace{\langle 0 \dots 0|}_n + e^{i\alpha} \underbrace{|1 \dots 1\rangle}_m \underbrace{\langle 1 \dots 1|}_n$

- $GreenSpider(0, 1)_0 = |0\rangle \cdot 1 + e^{i \cdot 0} |1\rangle \cdot 1 = \begin{bmatrix} 1 \\ 1 \end{bmatrix} \propto |+\rangle$

- $GreenSpider(0, 1)_\pi = |0\rangle \cdot 1 + e^{i \cdot \pi} |1\rangle \cdot 1 = \begin{bmatrix} 1 \\ -1 \end{bmatrix} \propto |-\rangle$

- **Z-Basis:**  $RedSpider(n, m)_\alpha = \underbrace{|+\dots+\rangle}_m \underbrace{\langle +\dots+|}_n + e^{i\alpha} \underbrace{|-\dots-\rangle}_m \underbrace{\langle -\dots-|}_n$

- $RedSpider(0, 1)_0 = |+\rangle \cdot 1 + e^{i \cdot 0} |-\rangle \cdot 1 = \begin{bmatrix} 2 \\ 0 \end{bmatrix} \propto |0\rangle$

- $RedSpider(0, 1)_\pi = |+\rangle \cdot 1 + e^{i \cdot \pi} |-\rangle \cdot 1 = \begin{bmatrix} 0 \\ 2 \end{bmatrix} \propto |1\rangle$

$$\textcircled{0} = |+\rangle$$

$$\textcircled{\pi} = |-\rangle$$

$$\textcircled{0} = |0\rangle$$

$$\textcircled{\pi} = |1\rangle$$

# Spiders for Pauli Matrices

- **Pauli-Z:**  $GreenSpider(n, m)_\alpha = \underbrace{|0 \dots 0\rangle}_m \underbrace{\langle 0 \dots 0|}_n + e^{i\alpha} \underbrace{|1 \dots 1\rangle}_m \underbrace{\langle 1 \dots 1|}_n$


- $GreenSpider(1, 1)_\pi = |0\rangle\langle 0| + e^{i\pi}|1\rangle\langle 1| = \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix} = Z$


- **Pauli-X:**  $RedSpider(n, m)_\alpha = \underbrace{|+\dots+\rangle}_m \underbrace{\langle +\dots+|}_n + e^{i\alpha} \underbrace{|-\dots-\rangle}_m \underbrace{\langle -\dots-|}_n$


- $RedSpider(1, 1)_\pi = |+\rangle\langle +| + e^{i\pi}|-\rangle\langle -| = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} = X$

- **Pauli-Y:**

- $RedSpider(1, 1)_\pi \circ GreenSpider(1, 1)_\pi = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix} \circ \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix} = \begin{bmatrix} 0 & -1 \\ 1 & 0 \end{bmatrix} \propto Y$

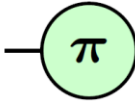
 = Z

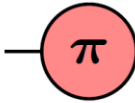 = X

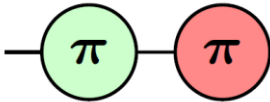  $\propto Y$

# Spider for Identity Matrix

- Every spider of arity 2 and phase angle  $\alpha = 0$  is an identity matrix
  - If spider has no angle, it implicitly means  $\alpha = 0$
  - $GreenSpider(1,1)_0 = |0\rangle\langle 0| + e^{i \cdot 0} |1\rangle\langle 1| = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = id_2$
  - $RedSpider(1,1)_0 = |+\rangle\langle +| + e^{i \cdot 0} |-\rangle\langle -| = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = id_2$
- This is an important rewrite rule!
  - Identity spiders can just be removed from the diagram

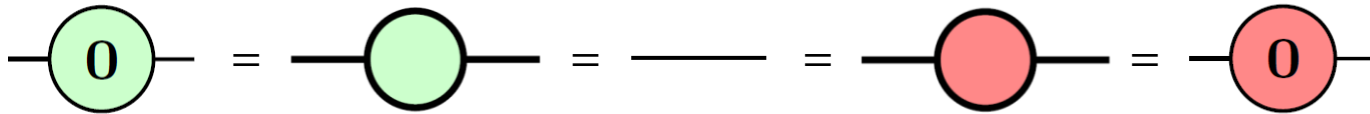


# Spider for Bell State

- Spiders can generate entangled States

$$- \text{GreenSpider}(0, 2)_0 = |00\rangle \cdot 1 + e^{i \cdot 0} |11\rangle \cdot 1 = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 1 \end{bmatrix} \propto |\Phi^+\rangle$$


- Using the identity rule from before we get a CAP
  - $|\Phi^+\rangle$  represent the Unit-Morphism from the compact monoidal category

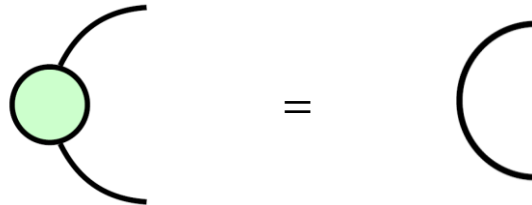



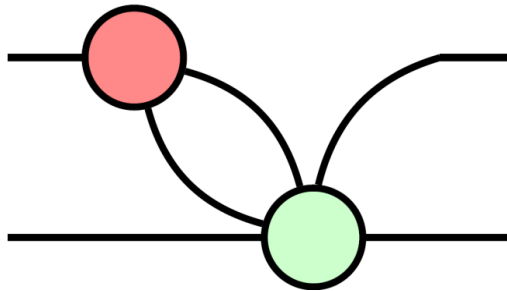
# Combining Spiders

- Bigger Graphs can be constructed by connecting spiders
  - Every output of a spider gets connected to the input of another spider
  - Again: Only Topology matters
- The resulting graph can represent a quantum circuit
  - But not every graph is a valid circuit


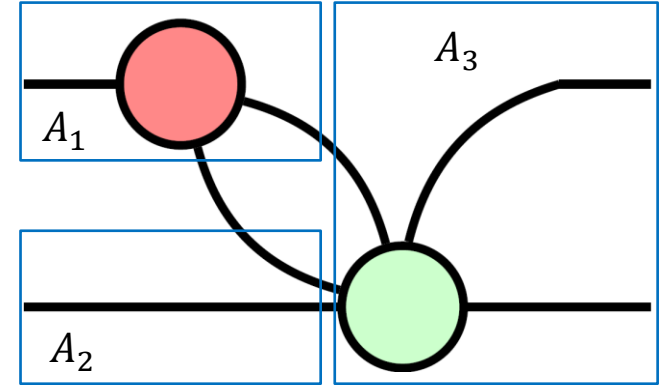
# Calculating a Graph

- To calculate the matrix representation
  - Divide the graph into regions
  - Each region must contain **exactly** one spider
- Simplification works just like normal circuits
  - “parallel” parts are combined using the tensor product
  - “sequential” parts are combined using the matrix product
- The resulting matrix represents the circuit
  - It is not necessary square / unitary




# Example: CNOT

## 1. Evaluate parallel Sections

- $A = A_1 \otimes A_2 = id_2 \otimes RedSpider(1,2)$
- $B = B_1 \otimes B_2 = GreenSpider(2,1) \otimes id_2$

## 2. Combine sequential Regions

- $CNOT = B \circ A$

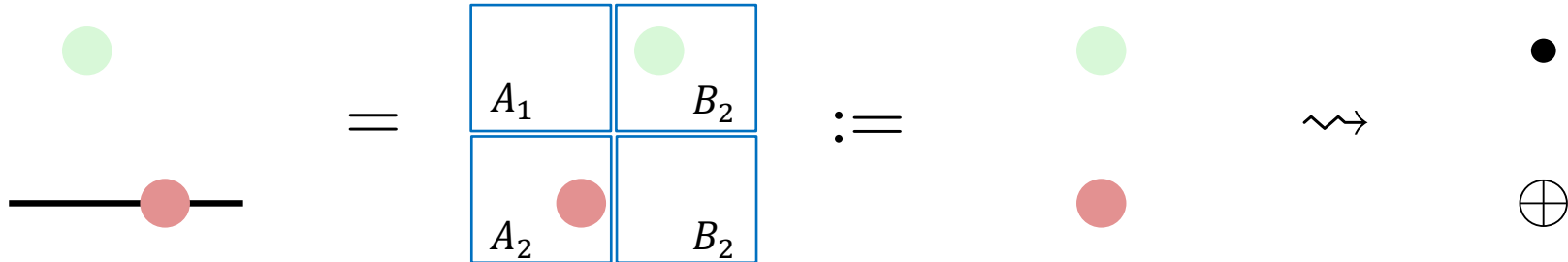


# Example: CNOT Parallel Sections

- $A = id_2 \otimes RedSpider(1,2) = id_2 \otimes (|+\rangle\langle+| + |-\rangle\langle-|)$

$$- A = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \otimes \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & 0 \\ 0 & 1 \\ 0 & 1 \\ 1 & 0 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$

- $B = GreenSpider(2,1) \otimes id_2 = (|00\rangle\langle 0| + |11\rangle\langle 1|) \otimes id_2$


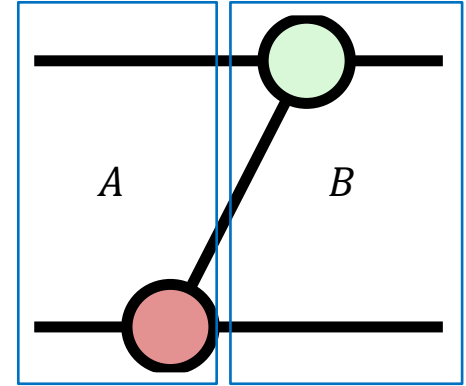
$$- B = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \otimes \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$


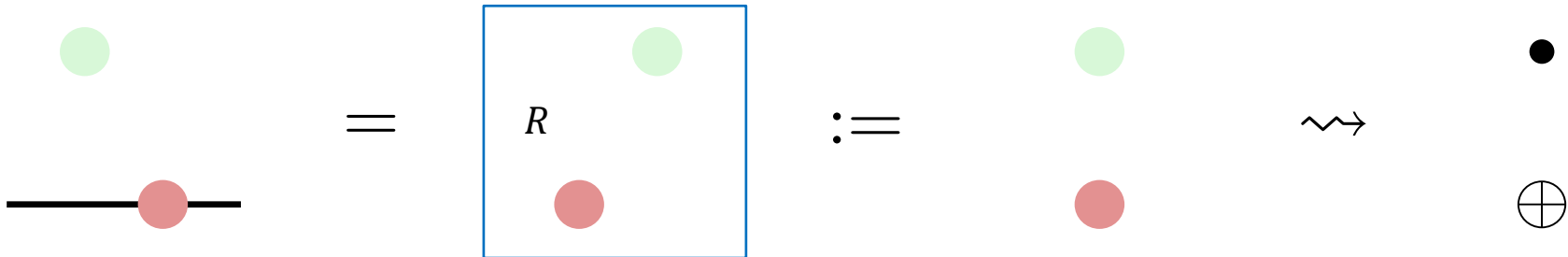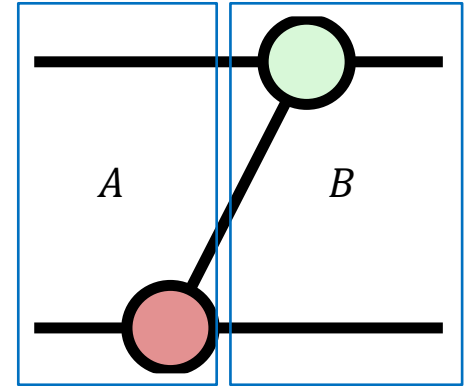
# Example: CNOT Sequential Sections


- $R = B \circ A$

$$- R = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \circ \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} \propto CNOT$$



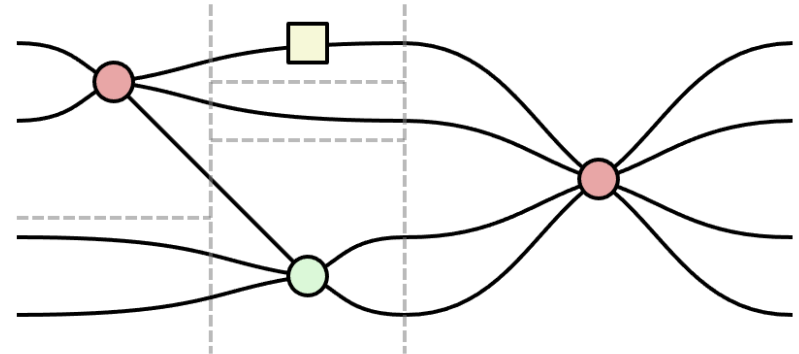
# Where to draw the Regions?

- There may exist multiple ways of drawing the regions
  - Obvious, as you are allowed to move components around
  - “Only topology matters”
- This leads to different matrices in the calculation process
  - But the final matrices are always equivalent
  - (neglecting the global scalar factor)
- But why do it this way?
  - It is just as bad as the classical matrix approach




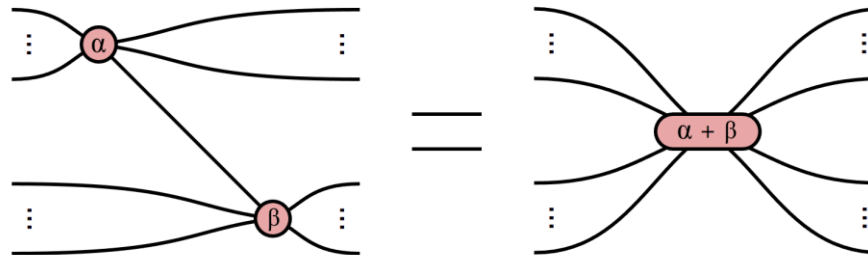
# Simplification Rules

- We don't want to calculate the graph using its matrix form
- There exist many rules to simplify ZX-Graphs
  - But far fewer rules as for classical circuits
- We can apply the rules anywhere in the graph if:
  - The pattern for the substitution matches
  - The order of the input / output wires of regions are unchanged
  - All rule still holds if the spiders flip colors


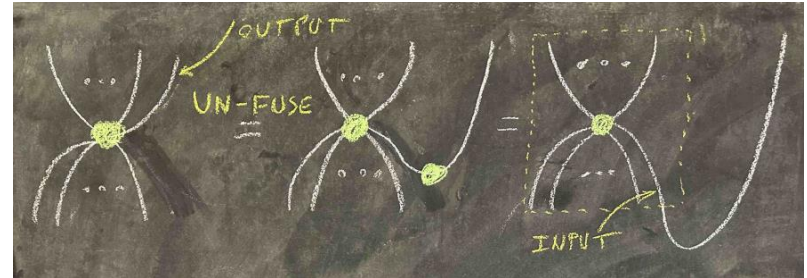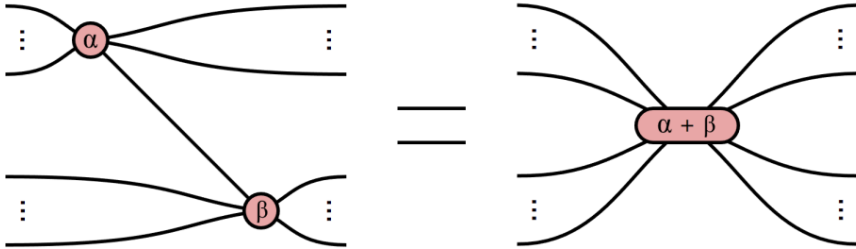
# Spider Fusion


- Idea: Two spiders of the same color fuse together
  - Phase angles add up
  - Can simplify graph a lot
- This rule allows to freely change input and outputs!
  - Only topology matters





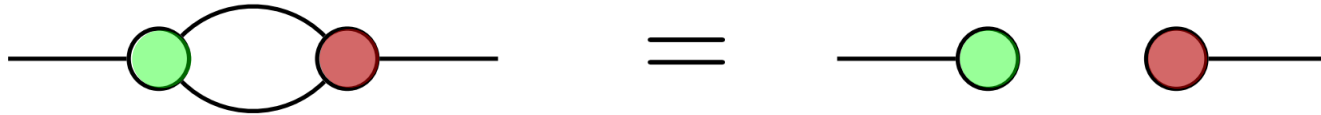
# Hopf Rule

- Idea: If two spiders of different color are connected by 2 lines, both lines can be deleted






# State Copy Rules

- Idea: “Green copies Red”, “Red copies Green”
  - Only works for computational basis states
    - $|0\rangle, |1\rangle / |+\rangle, |-\rangle$  depending on colors

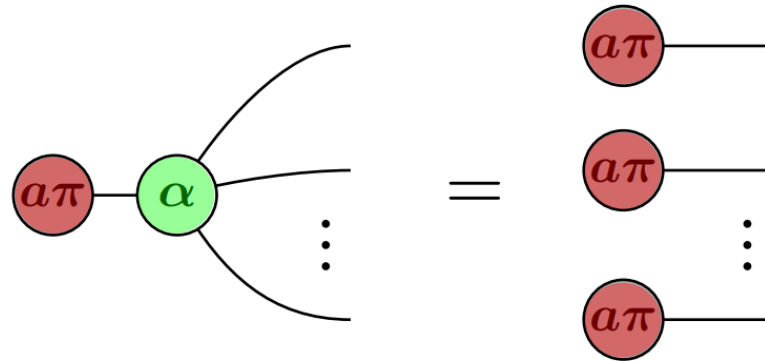

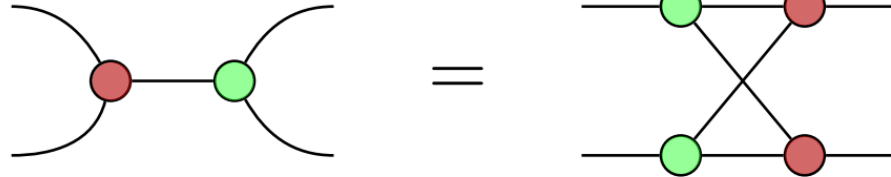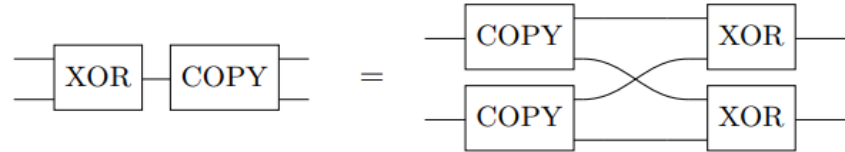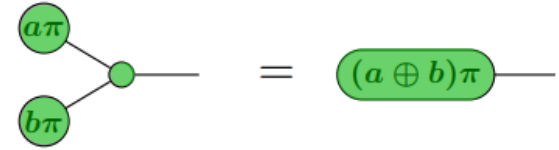
# Bi-Algebra Rule

- Analog to digital logic
  - Create XOR using spider fusion
  - Use Copy-Rule from before




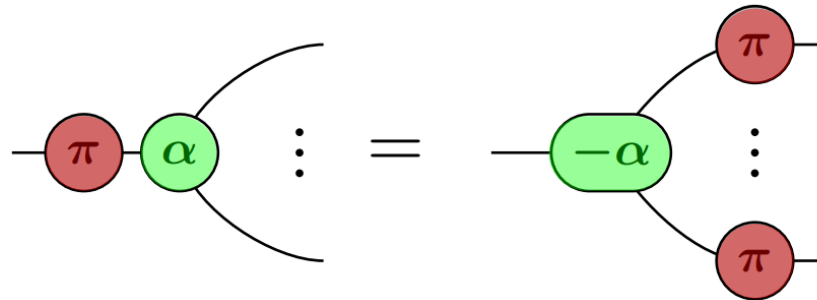- Idea: A spider with angle  $\pi$  copy through a spider of opposite color
  - The phase of the other spider gets flipped



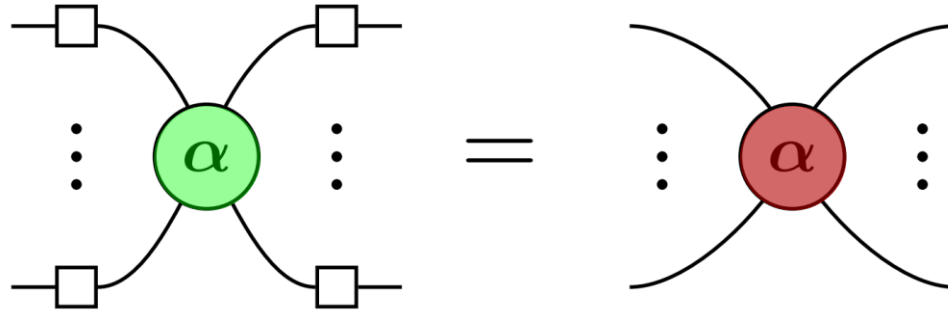
# Color Change Rule

- Idea: We can change the color of a single spider
  - But we need to add Hadamard gates to all its inputs / outputs to compensate
- Analog: A Hadamard Gate can push through a spider
  - By copying itself to every other output




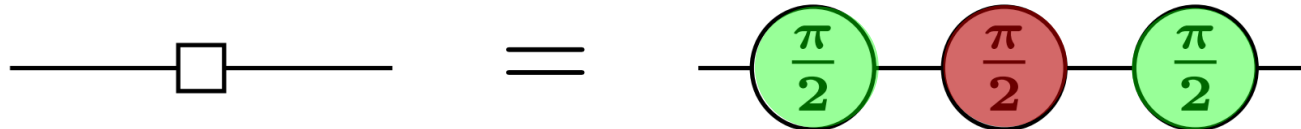
# Hadamard Gate

- Hadamard Gates can be constructed using euler angles
  - Set up Hadamard as sequence of rotations



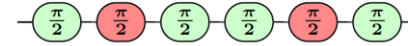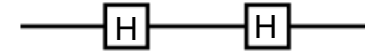
# Hadamard Gate Cancelation


- Two Hadamard Gates should cancel!
  - Using a visual proof, we see that the rule holds




(Translate to ZX)

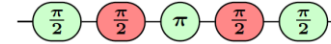


(Spider-Fusion)

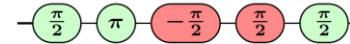

( $\pi$ -Commutation)

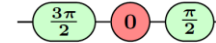

(Spider-Fusion)

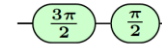

(Identity-Removal)



(Spider-Fusion)




(Modulo)



(Identity-Removal)

## Simplification: Three CNOTs




- Circuit containing 3 alternating CNOTs

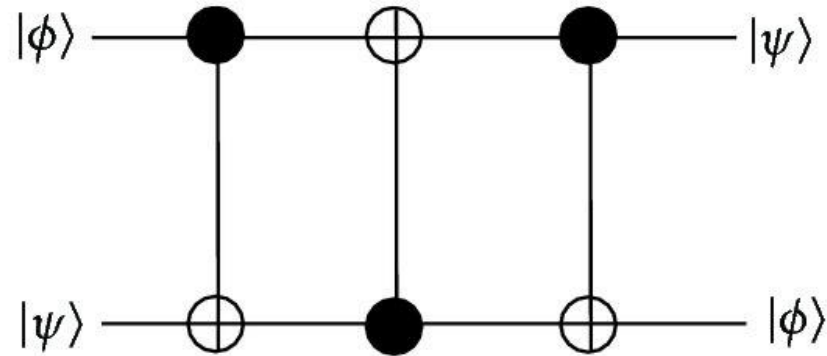



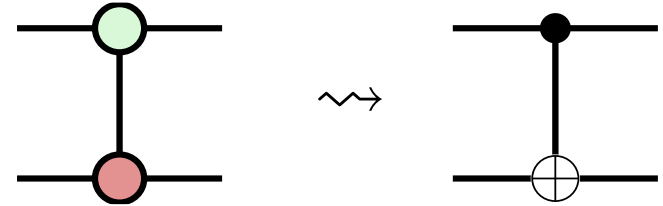
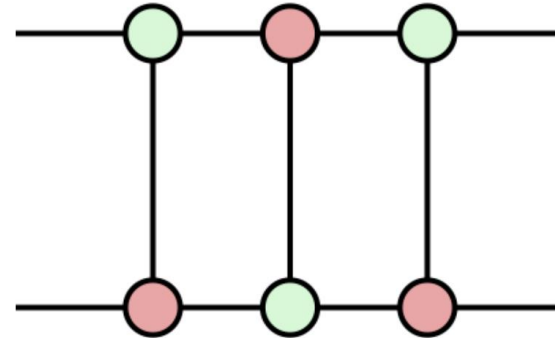
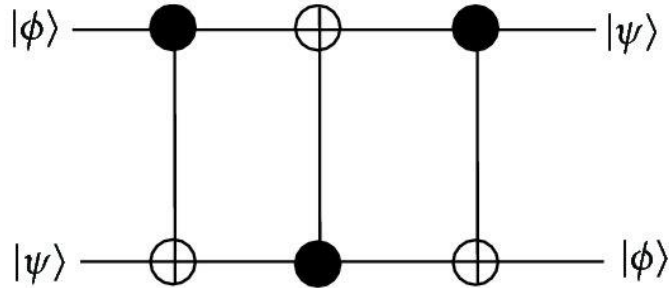
# Simplification: Three CNOTs

- Transform into ZX-Diagram
  - Remember CNOT Gate from earlier



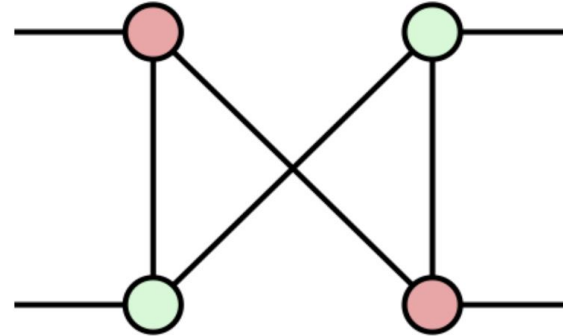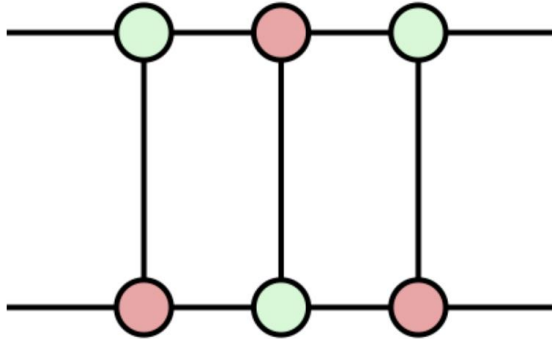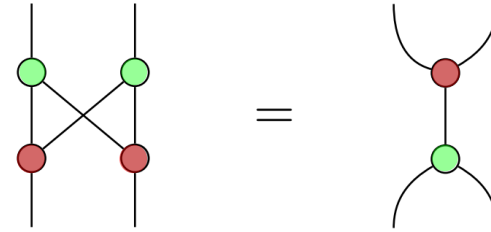
# Simplification: Three CNOTs

- Apply the bi-algebra rule
  - We need to morph the graph first!





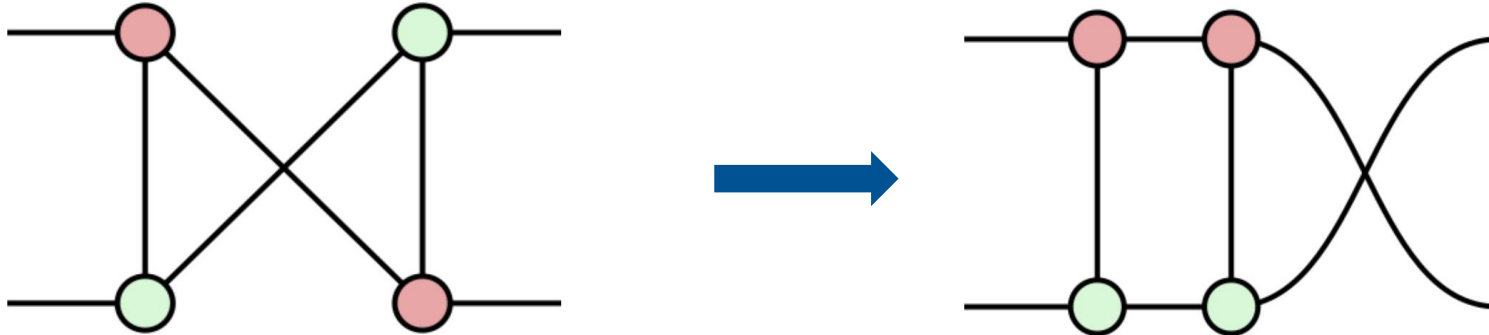
# Simplification: Three CNOTs

- Morph the ZX-Diagram
  - Allowed, since we are allowed to move stuff freely
  - Guaranteed by underlying category



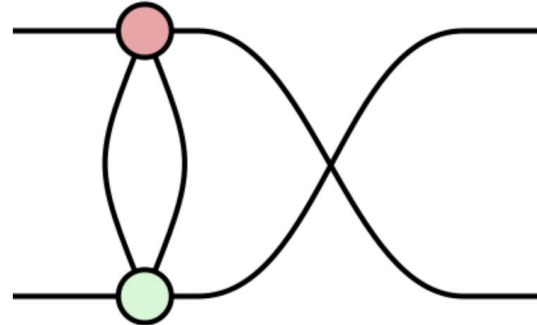
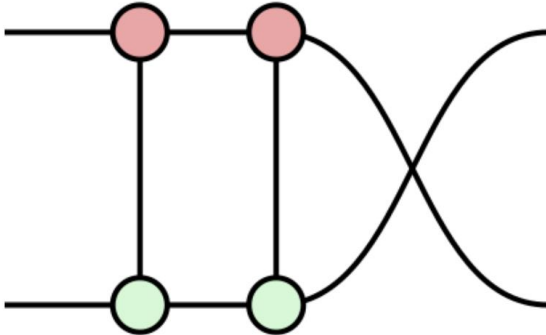
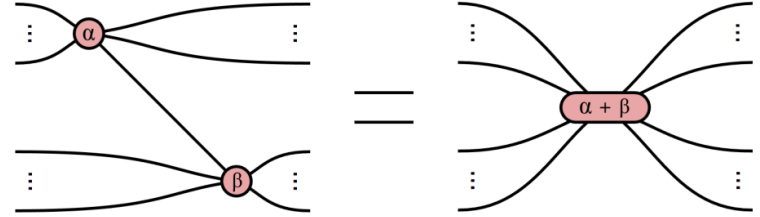
# Simplification: Three CNOTs

- Apply spider fusion rule
  - Attention, two wires remain between the first nodes!




# Simplification: Three CNOTs

- Apply the Hopf-Law

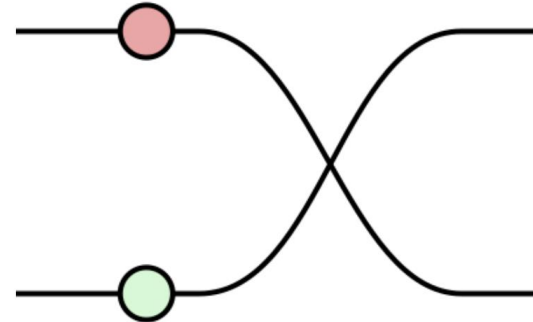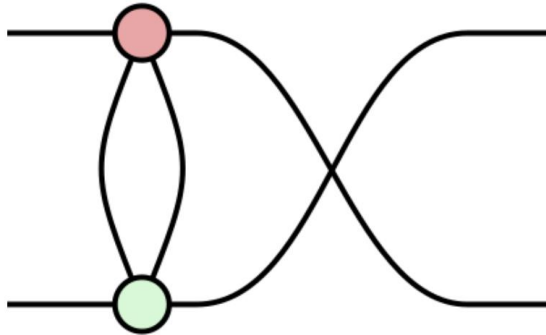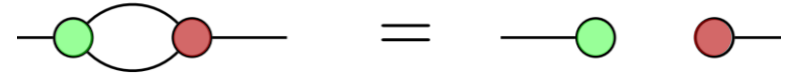



## Simplification: Three CNOTs

- Identity Removal

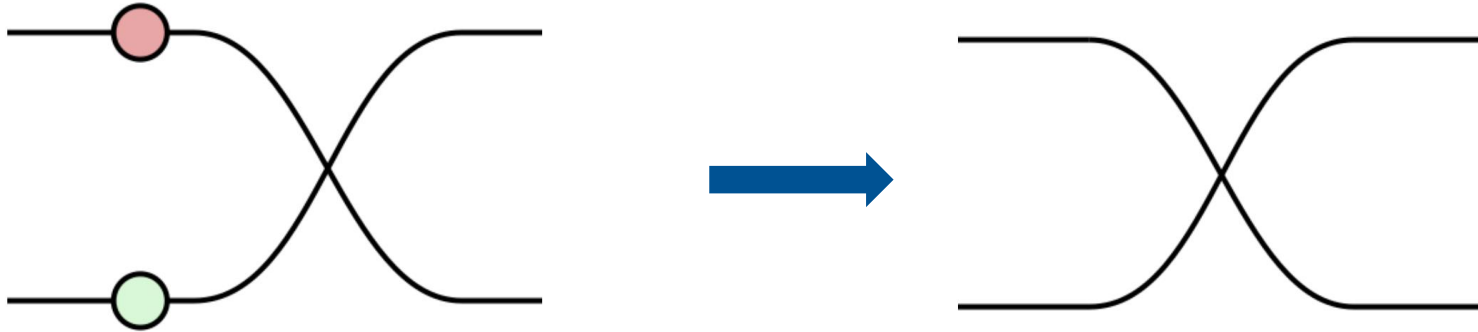
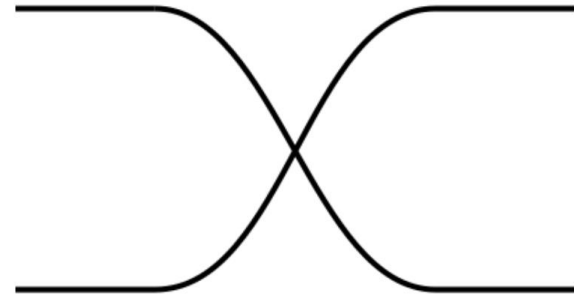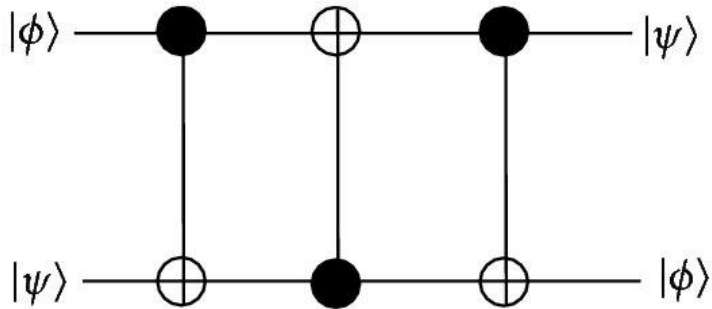
# Simplification: Three CNOTs


- Complicated CNOT circuit is actually a swap operation
  - Since we are working at the *atom*-level many other circuits can be simplified like this
  - Extracting back quantum circuits is hard
    - But it's possible for simple circuits
    - (In general: Graph needs to have “gFlow”)



# Translating Circuits

identity		$\begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$
Pauli Z		$\begin{pmatrix} 1 & 0 \\ 0 & -1 \end{pmatrix}$
Pauli X NOT gate		$\begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$
Pauli Y	$i$	$\begin{pmatrix} 0 & -i \\ i & 0 \end{pmatrix}$
Hadamard gate		$\frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$
S gate		$\begin{pmatrix} 1 & 0 \\ 0 & i \end{pmatrix}$
V gate		$\frac{1}{2} \begin{pmatrix} 1+i & 1-i \\ 1-i & 1+i \end{pmatrix}$
T gate		$\begin{pmatrix} 1 & 0 \\ 0 & e^{i\pi/4} \end{pmatrix}$

CNOT gate CX gate	$\sqrt{2}$	$\begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$
CZ gate	$\sqrt{2}$	$\begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 \end{pmatrix}$

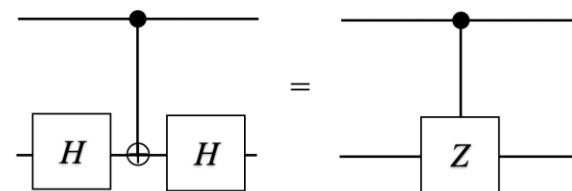


Challenge: Try to prove this identity!




# From Quantum Circuits to ZX-Diagrams

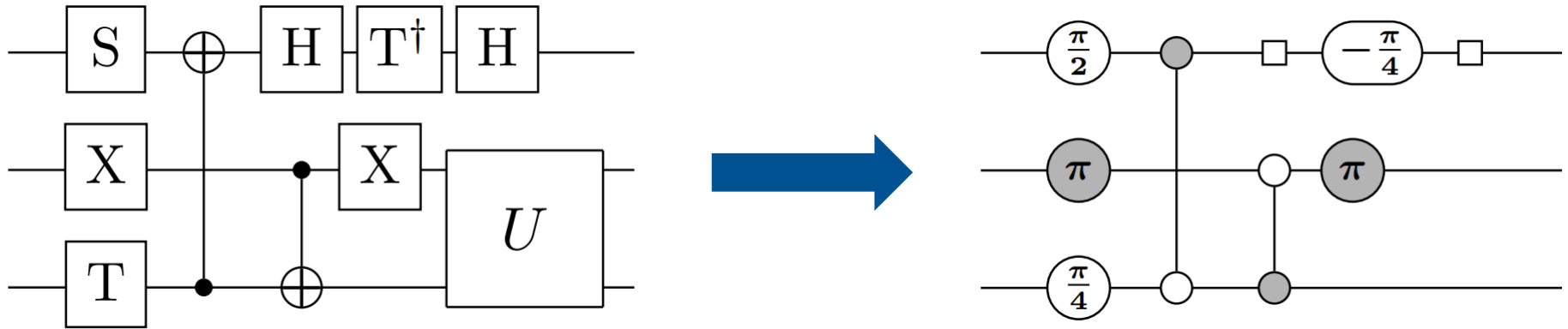- Example Circuit:
  - Custom gates need to be handled separately
- Backwards direction also possible




# Quantum Teleportation

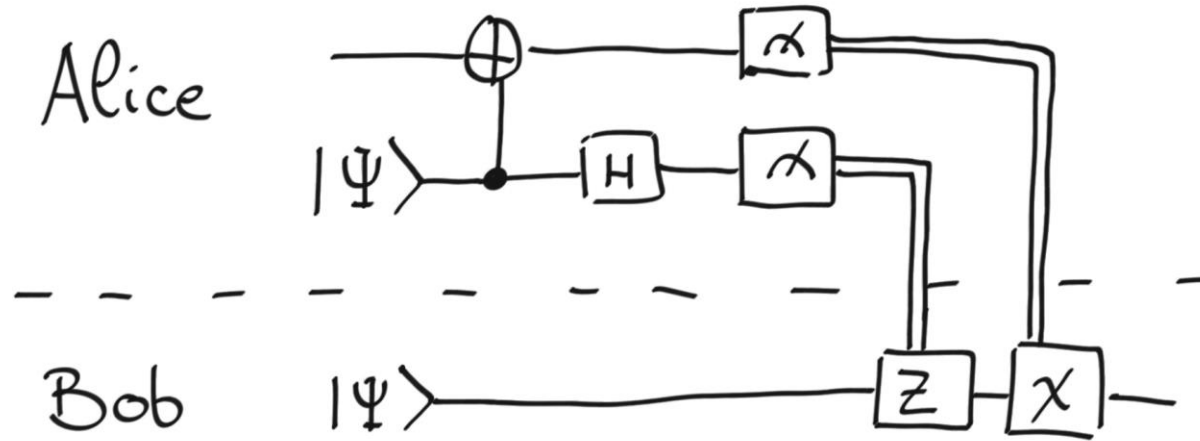

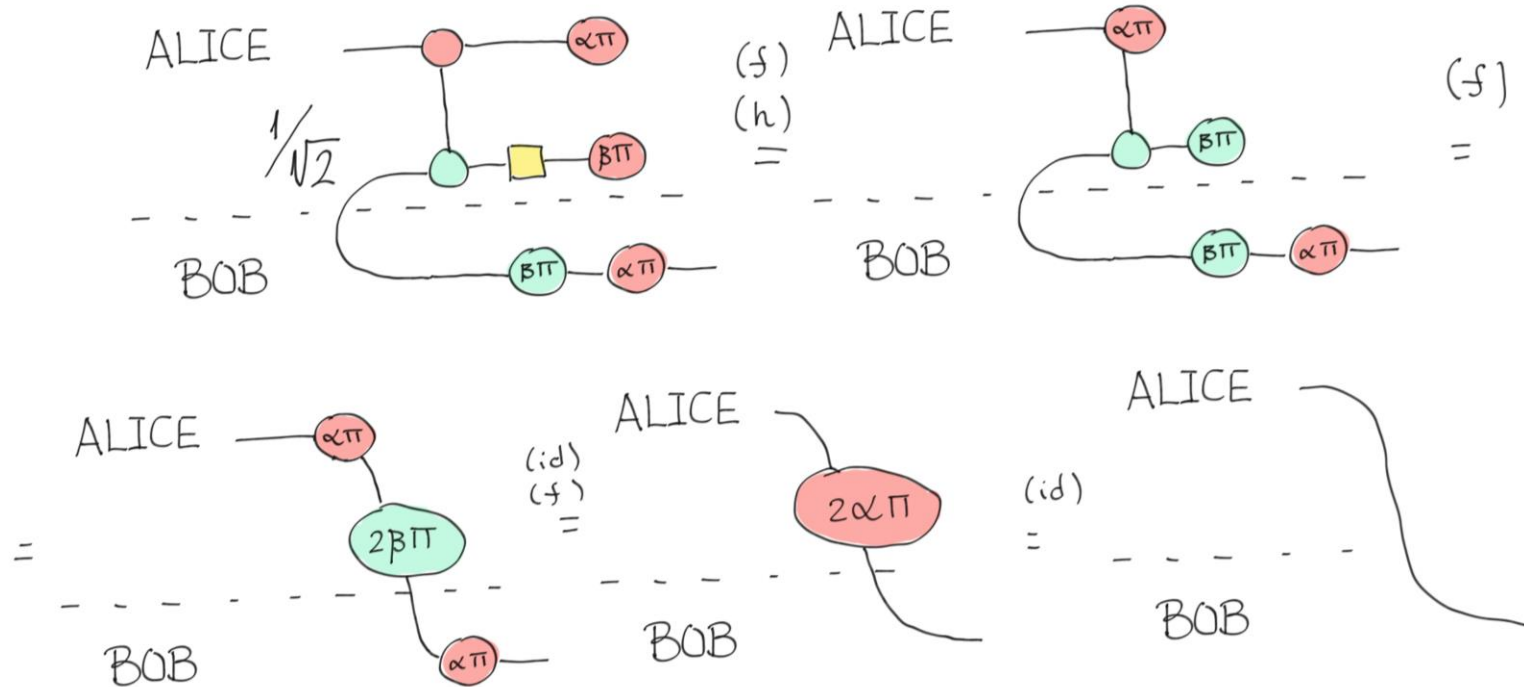
# Quantum Teleportation

- Shared Bell State, is just a bent wire!





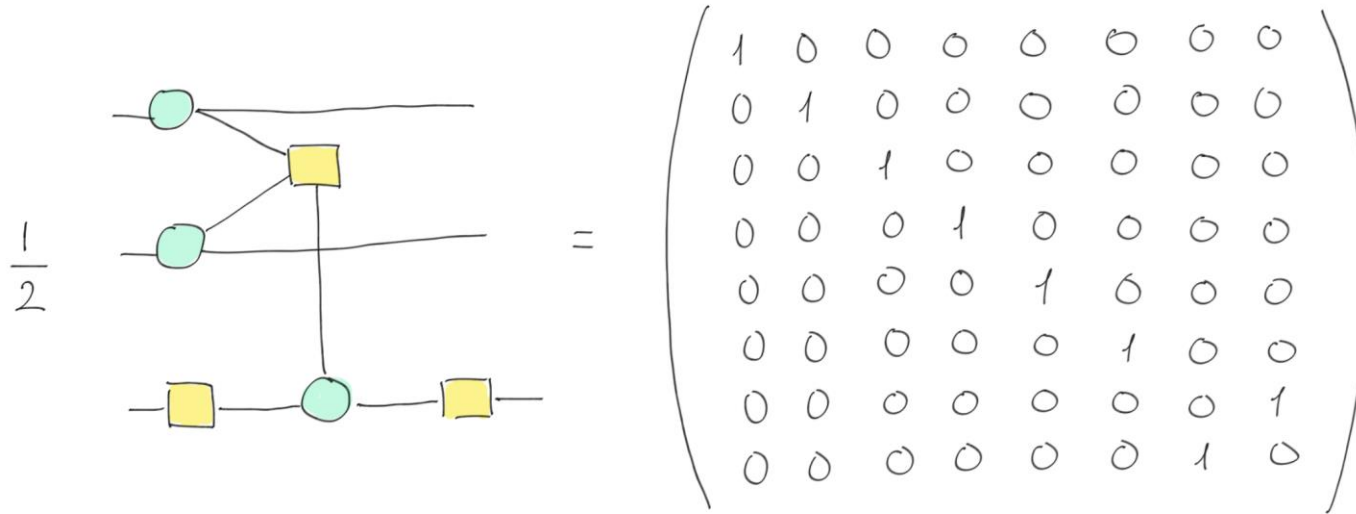
# Toffoli Gate

- Toffoli gate calculates a “quantum-AND” between two states
  - We introduced a new Generator: A “H-Box” to simplify the circuit. (Normally it has 25 Spiders)




# Toffoli Gate

- Toffoli Gate applied to  $|11\rangle$

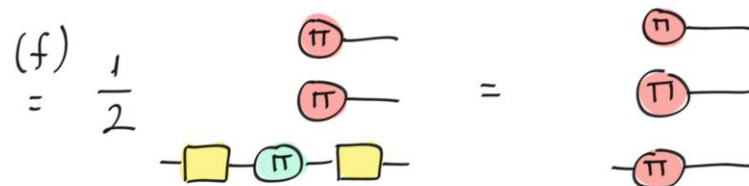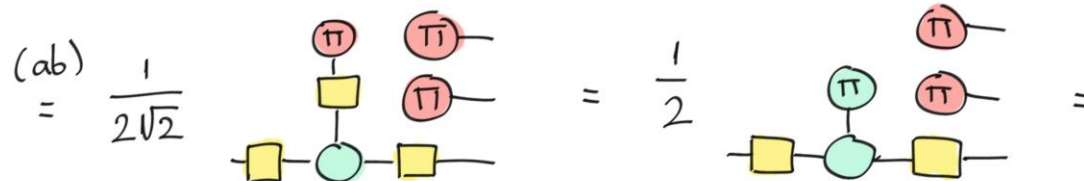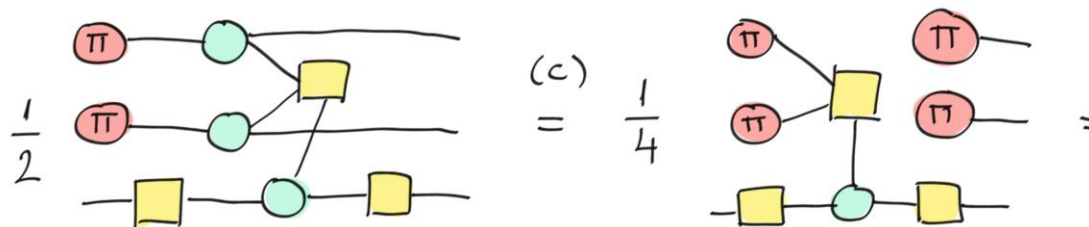

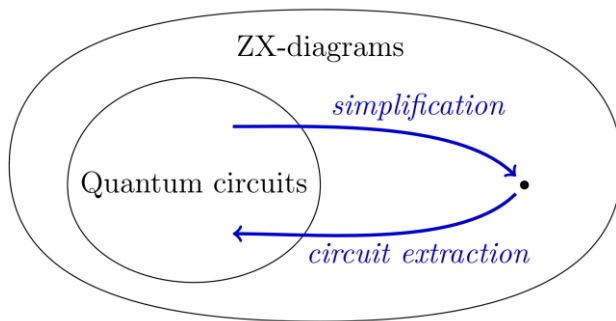- ZX Calculus is complete
  - Any two ZX-Graphs for the same Quantum circuit can be transformed into each other
  - By just using the rules from before!
- This means that if a simpler circuit exists, it can be found using ZX-calculus
  - But the path between those transformations may traverse invalid quantum circuits



- Circuit compilation: [https://www.cda.cit.tum.de/files/eda/2020\\_iscas\\_efficient\\_correct\\_compilation\\_quantum\\_circuits.pdf](https://www.cda.cit.tum.de/files/eda/2020_iscas_efficient_correct_compilation_quantum_circuits.pdf)
  - <https://quantum-journal.org/papers/q-2020-06-04-273/>
- Mathematical Background <https://www.youtube.com/watch?v=UQTTJV0eifw>
- Teleportation [https://pennylane.ai/qml/demos/tutorial\\_zx\\_calculus](https://pennylane.ai/qml/demos/tutorial_zx_calculus)

# Images

- Circuit optimization P.4: <https://quantum-journal.org/papers/q-2020-06-04-279/>
- Spider Fusion P.33: [https://www.cs.ox.ac.uk/people/bob.coecke/ZX-lectures\\_JPG.pdf](https://www.cs.ox.ac.uk/people/bob.coecke/ZX-lectures_JPG.pdf)